

ELEC 204 DIGITAL SYSTEM AND DESIGN

FINAL PROJECT REPORT

Student name: **Osman Raşit KÜLTÜR**

ID Number: **37250**

Instructor name: **Alper Tunga Erdoğan**

Project name: **Asynchronous Combination Lock**


Date: **12/05/2016**

INTRODUCTION

This combinational lock has a minimum sequence of four two-bit input symbols as the combination and appears to the user as if it is an asynchronous circuit. Actually, it is a synchronous circuit with a fast clock and synchronization of the user inputs. For a given input combination, the circuit goes to a state and cycles there until the input changes to a new symbol; thus, the combination cannot contain consecutive appearances of the same symbol. The lock is locked using an asynchronous RESET.

The project includes a D Flip Flop and Mealy State Diagram. The lock unlocks itself after entering four two-bit number in correct sequence. In this project we have assumed that it is 11100001. When each two-bit number specified correctly, corresponding LEDs will be turned on and if the user enter the 8-bit sequence correctly, all 8 LEDs will also be turned on. If the user makes a mistake in any state, the password has to be entered from the beginning. To unlock the circuit, the transitions between the states (given in the below) must be correct (from A to D means first to last). The D-Type Flip Flops save the inputs simultaneously with the manual clock to remember the old inputs. In this project, a manual clock is preferred instead of FPGA's clock.

STATE DIAGRAM

 

TRUTH TABLE

PRESENT STATE	INPUT	NEXT STATE
00	00	00
	01	10
	10	00
	11	00
01	00	00
	01	00
	10	11
	11	00
10	00	01
	01	00
	10	11
	11	00
11	00	01
	01	00
	10	00
	11	00

VHDL CODE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
-- My password is 11100001 in this case.
entity deneme is
    Port ( Clock : in  STD_LOGIC;
          Reset : in  STD_LOGIC;
          x1 : in  STD_LOGIC; -- MSB
          x0 : in  STD_LOGIC; -- LSB
          led1 : out STD_LOGIC;
          led2 : out STD_LOGIC;
          led3 : out STD_LOGIC;
          led4 : out STD_LOGIC;
          led5 : out STD_LOGIC;
          led6 : out STD_LOGIC;
          led7 : out STD_LOGIC;
          led8 : out STD_LOGIC);
end deneme;
architecture Behavioral of deneme is
    -- Intermediate Signals
    type state_type is (A,B,C,D);
    signal state : state_type;
```

Begin

-- If user enters wrong digits, the machine goes back to initial state. (goes state A)

process(Clock,Reset)

begin

if Reset='1' then state <=A;

elsif Clock'event and Clock='1' then

case state is

when A => if x1='1' and x0='1' then

state <= B;

else

state <= A;

end if;

when B => if x1='1' and x0='0' then

state <= C;

else

state <= A;

end if;

when C => if x1='0' and x0='0' then

state <= D;

else

state <= A;

end if;

```
when D => if x1='0' and x0='1' then
```

```
state <= A;
```

```
end if;
```

```
end case;
```

```
end if;
```

```
end process;
```

```
process(state,x1,x0)
```

```
begin
```

```
case state is
```

```
-- If first two digits are entered correctly, then first led will be on. Otherwise all leds are off.
```

```
when A => if x1='1' and x0='1' then
```

```
led1 <= '1';
```

```
led2 <= '0';
```

```
led3 <= '0';
```

```
led4 <= '0';
```

```
led5 <= '0';
```

```
led6 <= '0';
```

```
led7 <= '0';
```

```
led8 <= '0';
```

```
else
```

```
led1 <= '0';
```

```
led2 <= '0';
```

```
led3 <= '0';
```

```
led4 <= '0';
```

```
led5 <= '0';
```

```
led6 <= '0';
```

```
led7 <= '0';
```

```
led8 <= '0';
```

```
end if;
```

-- If second two digits are entered correctly, then first and second led will be on. Otherwise all leds are off.

when B => if x1='1' and x0='0' then

```
led1 <= '1';
```

```
led2 <= '1';
```

```
led3 <= '0';
```

```
led4 <= '0';
```

```
led5 <= '0';
```

```
led6 <= '0';
```

```
led7 <= '0';
```

```
led8 <= '0';
```

```
else
```

```
led1 <= '0';
```

```
led2 <= '0';
```

```
led3 <= '0';
```

```
led4 <= '0';
```

```
led5 <= '0';
```

```
led6 <= '0';
```

```
led7 <= '0';
```

```
led8 <= '0';
```

```
end if;
```

-- If third two digits are entered correctly, then first, second and third leds will be on. Otherwise all leds are off.

when C => if x1='0' and x0='0' then

```
led1 <= '1';
```

```
led2 <= '1';
```

```
led3 <= '1';
```

```
led4 <= '0';
```

```
led5 <= '0';
```

```
led6 <= '0';
```

```
led7 <= '0';
```

```
led8 <= '0';
```

```
else
```

```
led1 <= '0';
```

```
led2 <= '0';
```

```
led3 <= '0';
```

```
led4 <= '0';
```

```
led5 <= '0';
```

```
led6 <= '0';
```

```
led7 <= '0';
```

```
led8 <= '0';
```

```
end if;
```

-- If last two digits are entered correctly, then all eight leds will be on. Otherwise all leds are off.

when D => if x1='0' and x0='1' then

```
led1 <= '1';
```


```
led2 <= '1';
```


```
led3 <= '1';
```


```
led4 <= '1';
```

```
led5 <= '1';  
led6 <= '1';  
led7 <= '1';  
led8 <= '1';  
else  
led1 <= '0';  
led2 <= '0';  
led3 <= '0';  
led4 <= '0';  
led5 <= '0';  
led6 <= '0';  
led7 <= '0';  
led8 <= '0';  
end if;  
end case;  
end process;  
end Behavioral;
```


RTL SCHEMATICS

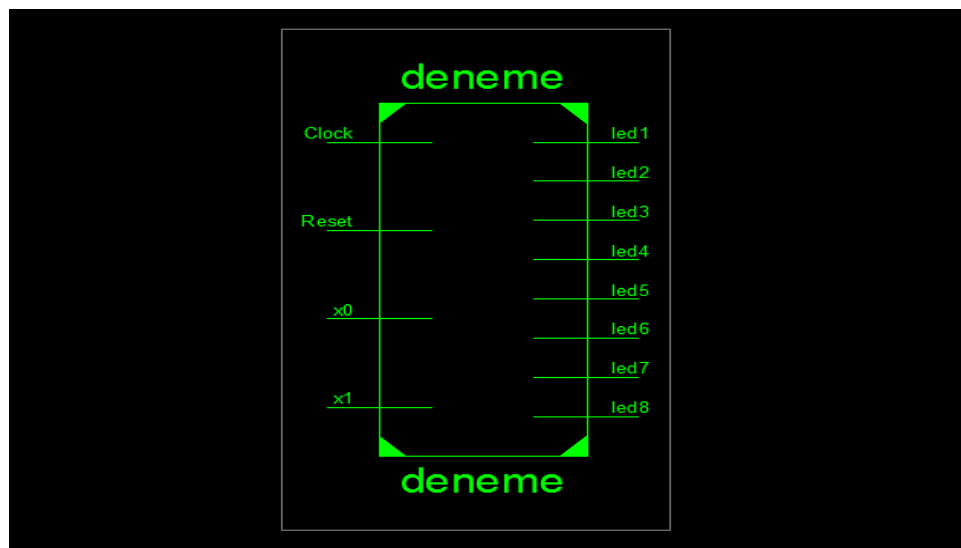

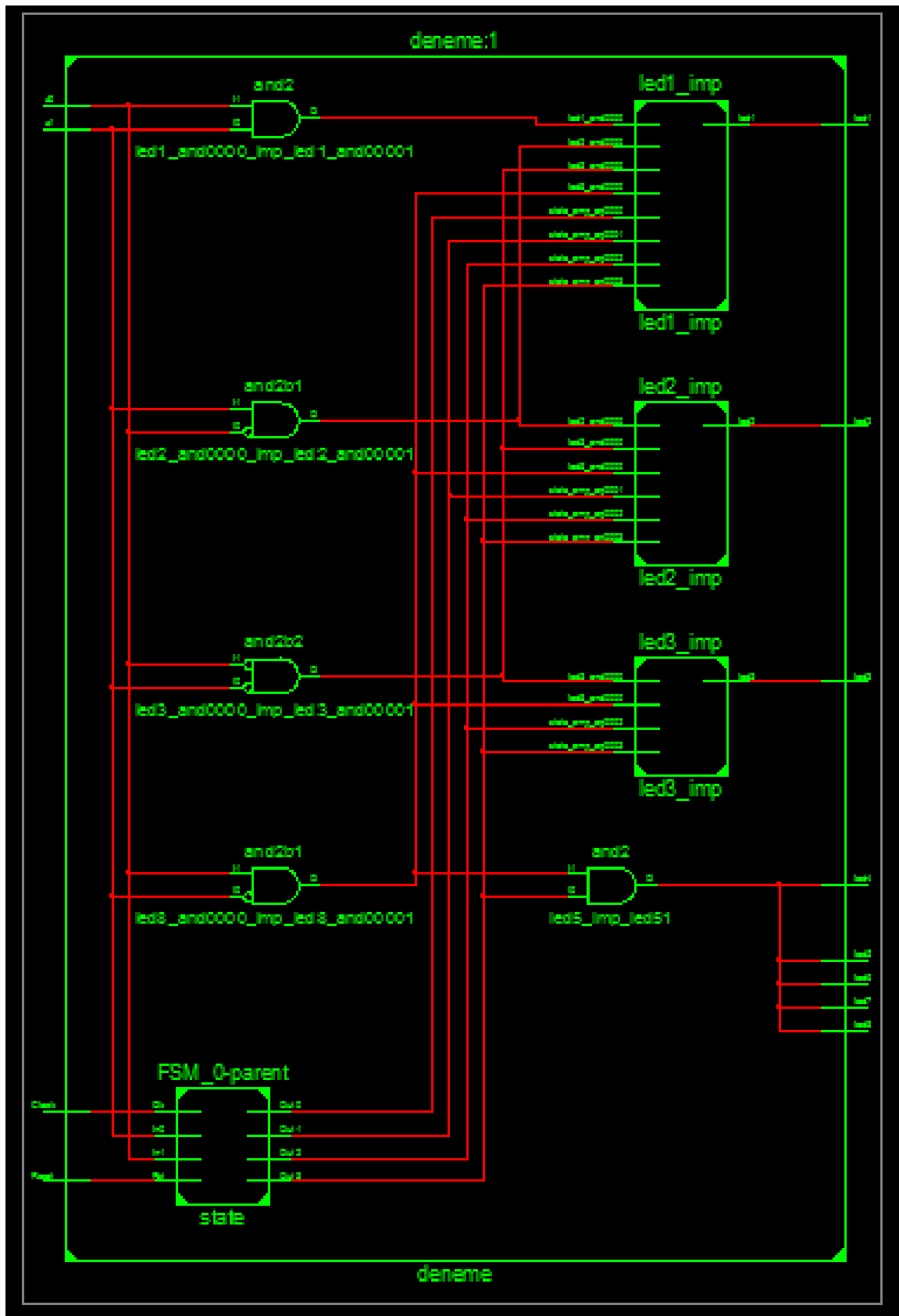

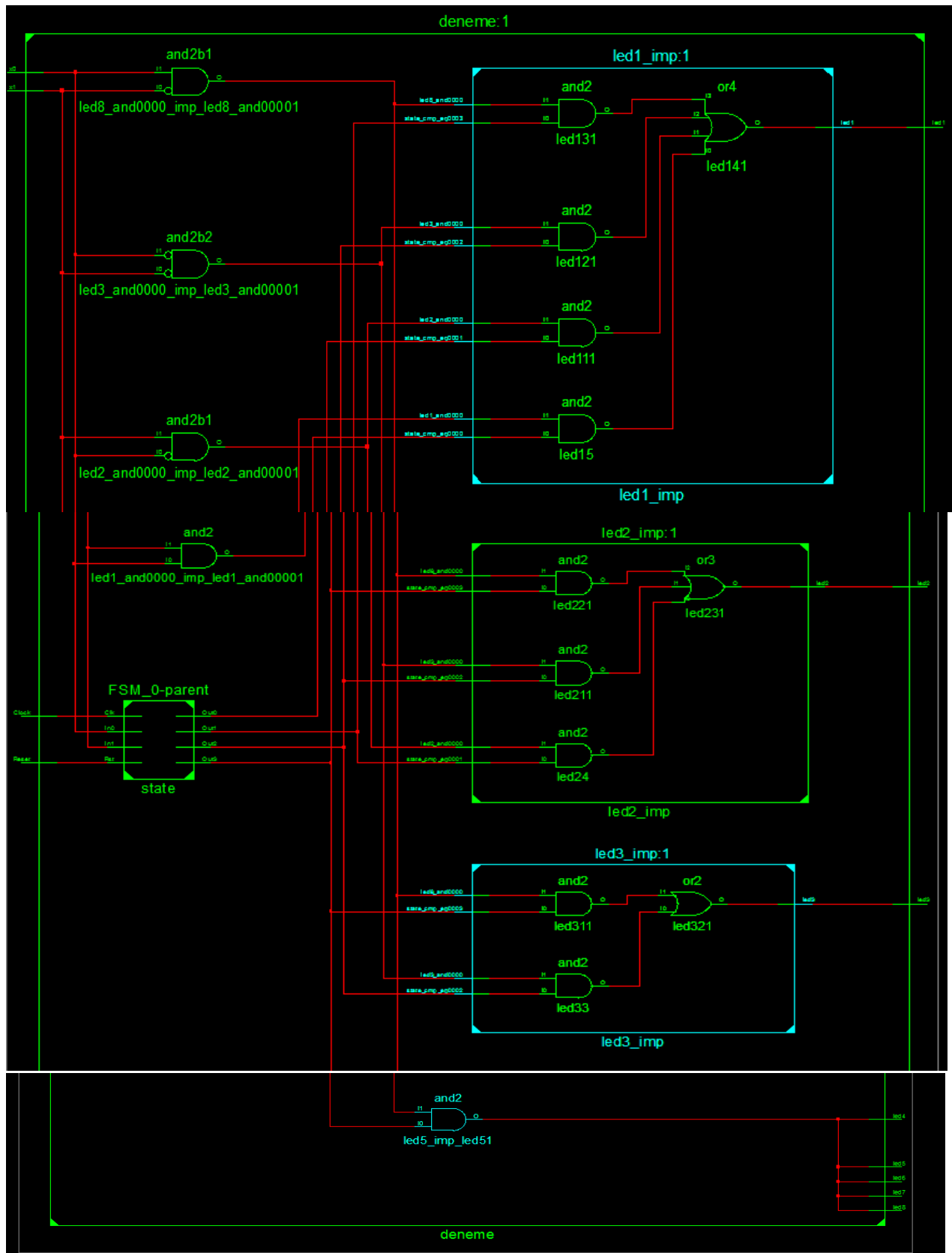

USER CONSTRAINTS

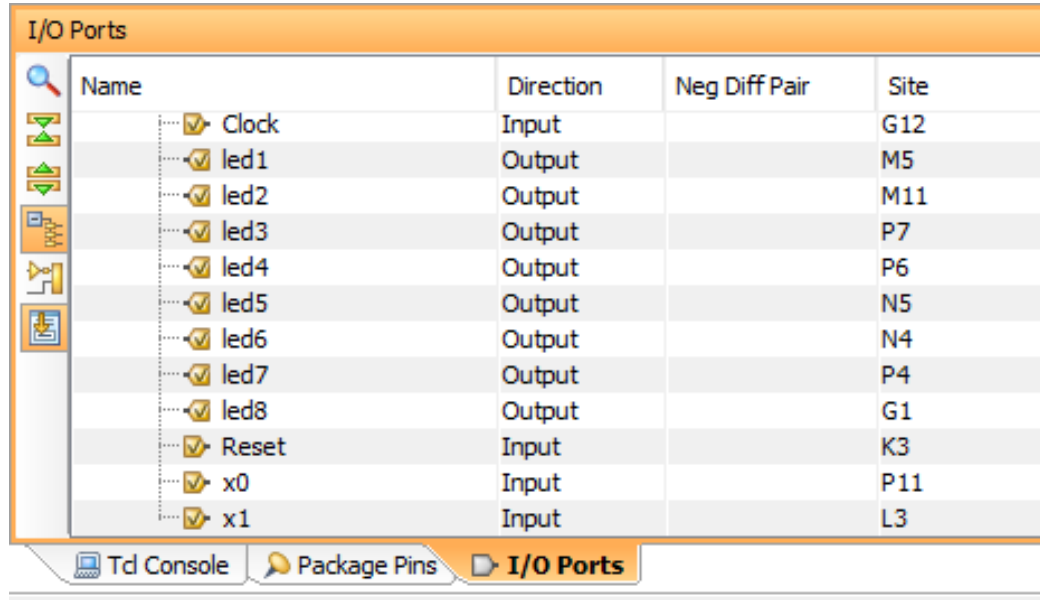

Name	Direction	Neg Diff Pair	Site
<input checked="" type="checkbox"/> Clock	Input		G12
<input checked="" type="checkbox"/> led1	Output		M5
<input checked="" type="checkbox"/> led2	Output		M11
<input checked="" type="checkbox"/> led3	Output		P7
<input checked="" type="checkbox"/> led4	Output		P6
<input checked="" type="checkbox"/> led5	Output		N5
<input checked="" type="checkbox"/> led6	Output		N4
<input checked="" type="checkbox"/> led7	Output		P4
<input checked="" type="checkbox"/> led8	Output		G1
<input checked="" type="checkbox"/> Reset	Input		K3
<input checked="" type="checkbox"/> x0	Input		P11
<input checked="" type="checkbox"/> x1	Input		L3

CONCLUSION

In this project, by using D-flip flops and state machines, I designed asynchronous combination lock. I used the development environment ISE 14.7 in my PC and ISE 10.1 in the lab. Rather than FPGA's itself clock, I have preferred to use manual clock to avoid any kind of frequency and time conflict. Syntax errors were pointed out by the ISE and I fixed them before the project presentation. As a result, we successfully unlocked the lock by entering 11100001 in a sequence. It is easy to change the password by changing a bit of code. By making this project and completing lab experiments, I'm convinced that I gained enough VHDL experience to do better jobs in the industry.